
NCCER ELECTRICAL LEVEL 2 – CONTROL SYSTEMS AND FUNDAMENTAL CONCEPTS (MODULE 26211-23) PRACTICE TEST (SAMPLE)

STUDY GUIDE

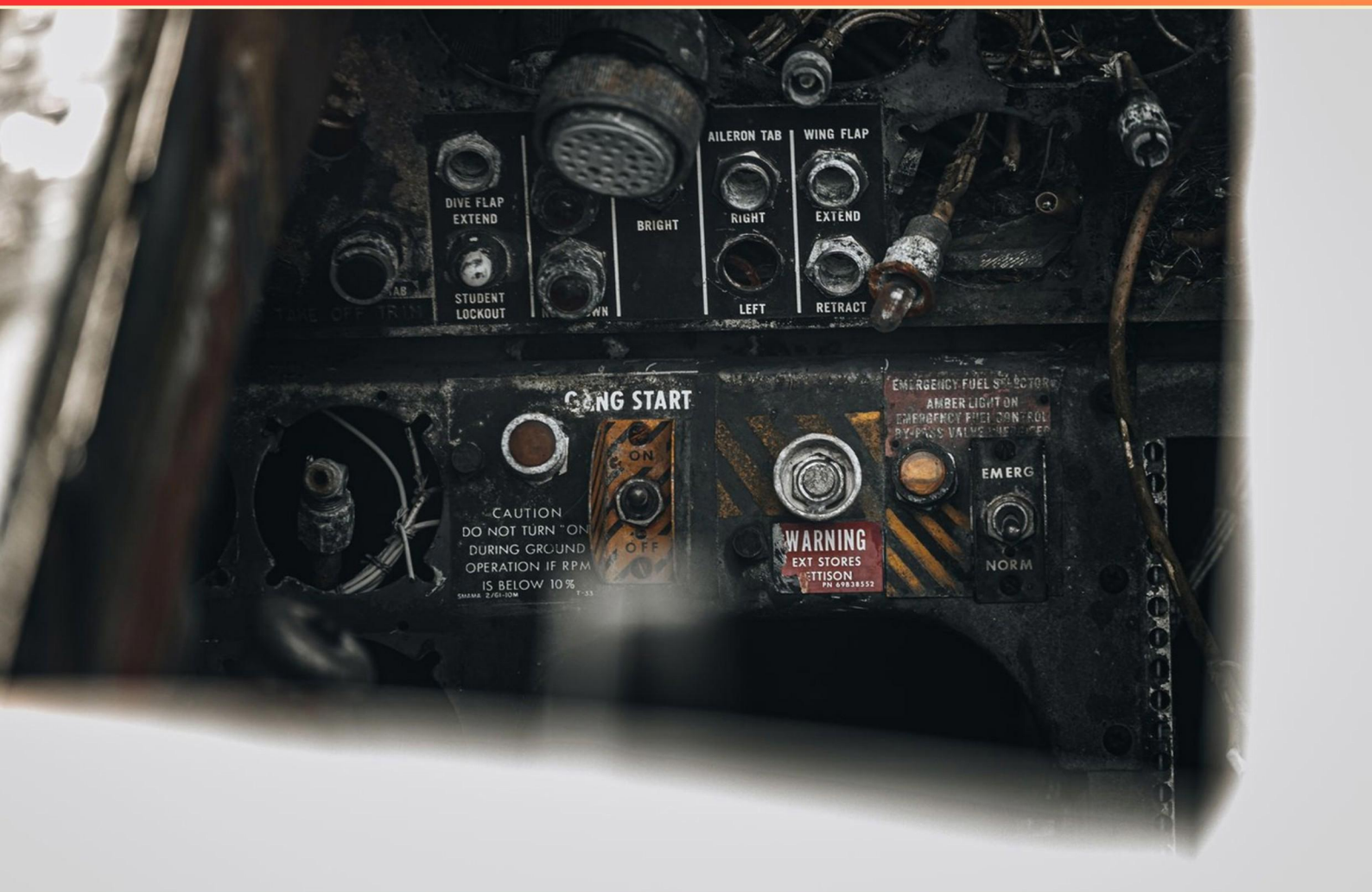

SAMPLE STUDY GUIDE WITH LIMITED QUESTIONS

VISIT US ONLINE FOR THE FULL VERSION STUDY GUIDE

https://nccerelectricallevel22621123.examzify.com

Copyright © 2026 by Examzify - A Kaluba Technologies Inc. product.

ALL RIGHTS RESERVED.

No part of this book may be reproduced or transferred in any form or by any means, graphic, electronic, or mechanical, including photocopying, recording, web distribution, taping, or by any information storage retrieval system, without the written permission of the author.

Notice: Examzify makes every reasonable effort to obtain accurate, complete, and timely information about this product from reliable sources.

SAMPLE

Table of Contents

Copyright 1
Table of Contents 2
Introduction 3
How to Use This Guide 4
Questions 5
Answers 8
Explanations 10
Next Steps 15

SAMPLE

Introduction

Preparing for a certification exam can feel overwhelming, but with the right tools, it becomes an opportunity to build confidence, sharpen your skills, and move one step closer to your goals. At Examzify, we believe that effective exam preparation isn't just about memorization, it's about understanding the material, identifying knowledge gaps, and building the test-taking strategies that lead to success.

This guide was designed to help you do exactly that.

Whether you're preparing for a licensing exam, professional certification, or entry-level qualification, this book offers structured practice to reinforce key concepts. You'll find a wide range of multiple-choice questions, each followed by clear explanations to help you understand not just the right answer, but why it's correct.

The content in this guide is based on real-world exam objectives and aligned with the types of questions and topics commonly found on official tests. It's ideal for learners who want to:

- Practice answering questions under realistic conditions,
- Improve accuracy and speed,
- Review explanations to strengthen weak areas, and
- Approach the exam with greater confidence.

We recommend using this book not as a stand-alone study tool, but alongside other resources like flashcards, textbooks, or hands-on training. For best results, we recommend working through each question, reflecting on the explanation provided, and revisiting the topics that challenge you most.

Remember: successful test preparation isn't about getting every question right the first time, it's about learning from your mistakes and improving over time. Stay focused, trust the process, and know that every page you turn brings you closer to success.

Let's begin.

SAMPLE

How to Use This Guide

This guide is designed to help you study more effectively and approach your exam with confidence. Whether you're reviewing for the first time or doing a final refresh, here's how to get the most out of your Examzify study guide:

1. Start with a Diagnostic Review

Skim through the questions to get a sense of what you know and what you need to focus on. Your goal is to identify knowledge gaps early.

2. Study in Short, Focused Sessions

Break your study time into manageable blocks (e.g. 30 – 45 minutes). Review a handful of questions, reflect on the explanations.

3. Learn from the Explanations

After answering a question, always read the explanation, even if you got it right. It reinforces key points, corrects misunderstandings, and teaches subtle distinctions between similar answers.

4. Track Your Progress

Use bookmarks or notes (if reading digitally) to mark difficult questions. Revisit these regularly and track improvements over time.

5. Simulate the Real Exam

Once you're comfortable, try taking a full set of questions without pausing. Set a timer and simulate test-day conditions to build confidence and time management skills.

6. Repeat and Review

Don't just study once, repetition builds retention. Re-attempt questions after a few days and revisit explanations to reinforce learning. Pair this guide with other Examzify tools like flashcards, and digital practice tests to strengthen your preparation across formats.

There's no single right way to study, but consistent, thoughtful effort always wins. Use this guide flexibly, adapt the tips above to fit your pace and learning style. You've got this!

SAMPLE

Questions

SAMPLE

1. What is one key benefit of performing a systematic test of a motor control circuit after changes?

A. It reduces risk of overlooking a fault and confirms safe operation

B. It guarantees no faults exist

C. It speeds up the motor start

D. It increases power efficiency

2. Fuses are not the best choice to provide motor overload protection because of the high inrush current when starting.

A. True

B. False

C. Only for DC applications

D. Fuses are the best choice for motor protection

3. What is the primary purpose of a bimetallic overload relay?

A. Protect motor by opening circuit during overload

B. Regulate motor speed

C. Filter electrical noise

D. Monitor power factor

4. Interlocking prevents both direction contactors from energizing at the same time.

A. Interlocking prevents energizing both direction contactors simultaneously, avoiding a direct short.

B. Allows energizing both direction contactors simultaneously for faster reversal.

C. Creates a direct short circuit if energized.

D. Does not affect circuit safety.

5. What is a holding contact in a control circuit and why is it used?

A. A holding contact is a fuse that protects the circuit.

B. A holding contact is a normally open or closed contact that maintains a circuit's state after the initiating device is released, providing a latch or self-hold.

C. A holding contact is a timer that delays release.

D. A holding contact is a lamp indicator.

SAMPLE

6. Emergency lighting circuits often use which type of relay so lamps can light instantly after a main power failure?

A. Magnetic Relays

B. Solid-State Relays

C. Reed Relays

D. Thermal Relays

7. Contractors are used to only MAKE and never BREAK the circuit to high-current, non-motor loads.

A. True

B. Sometimes

C. Not applicable

D. False

8. What is a timer relay and what are common types used in control circuits?

A. A timer relay provides a time delay before or after an input changes state.

B. A timer relay measures voltage

C. A timer relay outputs constant current

D. A timer relay reduces resistance

9. What is the function of a control transformer in control circuits?

A. To step down line voltage to control voltage and provide isolation.

B. To increase voltage for motors.

C. To convert AC to DC.

D. To supply power to the PLC memory.

10. Which statement correctly describes reversing the direction of a three-phase squirrel-cage motor?

A. You can reverse direction by swapping any two line leads (L1, L2, L3) with the corresponding motor terminals (T1, T2, T3).

B. Reversing direction requires swapping a specific pair of leads, not any two.

C. Direction reversal is achieved by swapping all three line leads.

D. Direction reversal is not possible in a three-phase motor.

SAMPLE

Answers

SAMPLE

1. A
2. A
3. A
4. A
5. B
6. A
7. D
8. A
9. A
10. B

SAMPLE

Explanations

SAMPLE

1. What is one key benefit of performing a systematic test of a motor control circuit after changes?

A. It reduces risk of overlooking a fault and confirms safe operation

B. It guarantees no faults exist

C. It speeds up the motor start

D. It increases power efficiency

Systematic testing after changes helps ensure safe operation by catching issues you might miss and confirming the circuit behaves correctly before it handles real loads. By stepping through the control circuit methodically, you verify wiring matches the schematic, confirm correct coil voltages and interlocks, validate the start/stop sequence, and test safety features like overload protection and emergency stops. This approach reduces the chance of an overlooked fault and gives confidence that the motor control will operate safely under normal and fault conditions. It's important to note that testing this way does not guarantee that no faults exist—some problems may only appear under load or after extended operation. It also isn't meant to promise faster starts or greater efficiency; its primary goal is safety and correct operation after changes.

2. Fuses are not the best choice to provide motor overload protection because of the high inrush current when starting.

A. True

B. False

C. Only for DC applications

D. Fuses are the best choice for motor protection

When protecting a motor, the control system needs to respond to overheating caused by overload, not just to brief current spikes. A motor draws a large inrush current when starting—often several times the running current. Fuses are mainly for short circuit protection and they melt after their current exceeds a rating for a certain time. That means using a fuse to handle motor overload can be problematic: if the fuse is sized to tolerate the startup surge, it won't reliably trip on an actual overload; if it's sized to protect against overload, it may nuisance trip during normal startup. So fuses aren't well-suited to provide proper motor overload protection. In practice, motors are protected by devices designed for motor overload, such as thermal or electronic overload relays (often in combination with fuses that handle short-circuit protection).

3. What is the primary purpose of a bimetallic overload relay?

A. Protect motor by opening circuit during overload

B. Regulate motor speed

C. Filter electrical noise

D. Monitor power factor

The main purpose is to protect the motor by opening the circuit when it overheats due to an overload. A bimetallic overload relay uses a strip made of two metals with different thermal expansion rates. When current heats the strip, it bends after reaching a set temperature, which trips the relay contacts or de-energizes the contactor coil. That interruption removes power to the motor, preventing damage from overheating. There's usually a built-in time delay to avoid nuisance trips from brief surges. This device protects against overload and stall, not speed control, noise filtering, or power-factor monitoring.

SAMPLE

4. Interlocking prevents both direction contactors from energizing at the same time.

A. Interlocking prevents energizing both direction contactors simultaneously, avoiding a direct short.

B. Allows energizing both direction contactors simultaneously for faster reversal.

C. Creates a direct short circuit if energized.

D. Does not affect circuit safety.

In a motor control circuit, interlocking is used to ensure only one direction contactor can be energized at a time. This prevents a direct short and protects both the electrical circuit and the mechanical system. How it works: a normally closed interlock contact from one direction path is wired in series with the coil of the opposite direction contactor. When the forward contactor is energized, its interlock contact opens the circuit to the reverse coil, so the reverse cannot energize. If someone tries to energize the reverse path, the forward interlock opens that circuit as well, blocking both from being on at once. Why this is best: it directly addresses the safety and reliability concern of having both direction coils energized simultaneously, which would create a dangerous condition and potential equipment damage. The alternative that suggests energizing both for faster reversal ignores the risk of a short and is not how these systems are designed. The idea that it creates a direct short if energized is the hazard interlock is meant to prevent, not a description of its normal function. And saying it doesn't affect circuit safety falsely ignores the protective purpose of the interlock.

5. What is a holding contact in a control circuit and why is it used?

A. A holding contact is a fuse that protects the circuit.

B. A holding contact is a normally open or closed contact that maintains a circuit's state after the initiating device is released, providing a latch or self-hold.

C. A holding contact is a timer that delays release.

D. A holding contact is a lamp indicator.

Holding contact is an auxiliary contact, usually the relay's own contact, that keeps the circuit energized after the initiating device is released, creating a latch or self-hold. In a typical start-stop control, pressing a momentary start pushbutton energizes the relay coil. The relay's normally open holding contact closes and provides a path around the start button, so when you release the start button, current still flows to the coil and the relay stays energized. A stop pushbutton (normally closed) in series will interrupt this path to de-energize when pressed. This arrangement lets the circuit stay on without you having to hold the button down and provides reliable, continuous operation. Other options don't fit because a fuse provides protection, not holding the circuit; a timer delays release rather than maintaining the state; and a lamp indicator shows status but does not keep the circuit energized.

SAMPLE

6. Emergency lighting circuits often use which type of relay so lamps can light instantly after a main power failure?

A. Magnetic Relays

B. Solid-State Relays

C. Reed Relays

D. Thermal Relays

Instantly switching on power loss requires a control device that acts like a fast, fail safe mechanical switch. Magnetic relays fit this need because they use an electromagnet to move a contact set, delivering a quick, reliable changeover when the power state changes. In an emergency lighting circuit, the sensing logic keeps the normal path energized while power is present; when the main supply fails, the coil loses power and the spring returns the contacts to the emergency path, routing the lamps to the battery/inverter immediately. This simple, robust behavior makes magnetic relays ideal for switching high-current lighting loads without delay. Solid state relays can switch fast but may introduce leakage current and heat management concerns in lighting circuits. Reed relays are typically used for small signals, not heavy lighting loads. Thermal relays are slow because they rely on heating to operate, so they would not meet the requirement for immediate activation.

7. Contractors are used to only MAKE and never BREAK the circuit to high-current, non-motor loads.

A. True

B. Sometimes

C. Not applicable

D. False

Contractors are devices that control power to a load by closing and opening the main contacts. When the control coil is energized, the contacts close and complete the circuit (make), allowing current to flow to the load. When the coil is de-energized, the contacts open and interrupt the circuit (break), stopping current. So, for high-current, non-motor loads, the purpose isn't limited to just making the circuit; they are designed to both make and break the circuit as part of turning the load on and off. Proper ratings and arc suppression are important, but the fundamental function includes breaking the circuit as well as making it.

8. What is a timer relay and what are common types used in control circuits?

A. A timer relay provides a time delay before or after an input changes state.

B. A timer relay measures voltage

C. A timer relay outputs constant current

D. A timer relay reduces resistance

A timer relay creates a controlled time delay in a control circuit, delaying either the energizing or the de-energizing of a load after an input changes state. This lets you sequence actions, prevent nuisance or chatter from rapid changes, and give equipment time to stabilize during start-up or shut-down. In practice you'll see two main timing actions: delay after the input is energized before the output activates (delay-on-make), and a delay after the input is removed before the output deactivates (delay-on-break). Timer relays come in electromechanical varieties, which use a small motor or clockwork and adjust the delay with a dial or preset, and solid-state varieties, which use digital circuitry to produce precise delays and often offer multiple timing ranges. Some timers also function as one-shot (produces a single pulse when triggered) or interval types (repeated pulses). These devices are chosen for control circuits to achieve proper sequencing, smoother startups, and safer, more reliable operation.

SAMPLE

9. What is the function of a control transformer in control circuits?

A. To step down line voltage to control voltage and provide isolation.

B. To increase voltage for motors.

C. To convert AC to DC.

D. To supply power to the PLC memory.

A control transformer steps down incoming line voltage to a lower, safe control voltage and provides isolation between the power and control circuits. This lower voltage powers control devices like relays, contactors, timers, and PLC input modules, while the isolation helps protect personnel and equipment from faults on the power side and reduces electrical noise in the control circuit. It doesn't raise voltage for motors, nor does it convert AC to DC (that's a rectifier), and while PLCs use low voltage, their memory is typically supplied by a dedicated DC power supply rather than directly by the transformer.

10. Which statement correctly describes reversing the direction of a three-phase squirrel-cage motor?

A. You can reverse direction by swapping any two line leads (L1, L2, L3) with the corresponding motor terminals (T1, T2, T3).

B. Reversing direction requires swapping a specific pair of leads, not any two.

C. Direction reversal is achieved by swapping all three line leads.

D. Direction reversal is not possible in a three-phase motor.

The key idea is that the rotation of a three-phase motor is set by the order of the three phase voltages applied to the windings. If you interchange two of the supply lines, you change the phase sequence (for example from A-B-C to A-C-B), which flips the direction of the rotating magnetic field and thus reverses the motor's rotation. You don't need to swap a specific predetermined pair—any two of the three lines will produce reversal. Swapping all three lines leaves the sequence effectively unchanged, so it won't reverse direction. Reversing a three-phase squirrel-cage motor is indeed possible by changing the phase sequence.

SAMPLE

Next Steps

Congratulations on reaching the final section of this guide. You've taken a meaningful step toward passing your certification exam and advancing your career.

As you continue preparing, remember that consistent practice, review, and self-reflection are key to success. Make time to revisit difficult topics, simulate exam conditions, and track your progress along the way.

If you need help, have suggestions, or want to share feedback, we'd love to hear from you. Reach out to our team at hello@examzify.com.

Or visit your dedicated course page for more study tools and resources:

https://nccerelectricallevel22621123.examzify.com

We wish you the very best on your exam journey. You've got this!

SAMPLE